

## Chapter 3

# Modeling and Control of DC-DC Converters

Yanfeng Shen<sup>\*</sup>, Zian Qin<sup>†</sup> and Huai Wang<sup>\*</sup>

<sup>\*</sup>Aalborg University, Aalborg, Denmark, <sup>†</sup>Delft University of Technology, Delft, The Netherlands

### 3.1 FREQUENCY-DOMAIN VOLTAGE-MODE CONTROL OF A BUCK DC-DC CONVERTER

#### 3.1.1 Specifications of the Buck DC-DC Converter

The circuit diagram of the Buck DC-DC converter is shown in Fig. 3.1. The input voltage  $V_{in}=110\text{ V}$ , the output voltage  $V_o=48\text{ V}$ , the nominal output power  $P_{oN}=500\text{ W}$ , the switching frequency  $f_s=100\text{ kHz}$ , the maximum current ripple in the output inductor  $\Delta I_{Lo}=10\% I_o$ , and the maximum output voltage ripple  $\Delta V_o=0.5\% V_o$ . For an output voltage of  $48\text{ V}$ , the corresponding duty cycle  $D=V_o/V_{in}=48\text{ V}/110\text{ V}=0.44$  and the output current  $I_o=500\text{ W}/48\text{ V}=10.42\text{ A}$ . Based on the specifications, the required output inductance  $L_o$  and output capacitance  $C_o$  can be obtained

$$L_o \geq \frac{(1-D)T_s V_o}{\Delta I_{Lo}} = \frac{(1-0.44) \times 10 \times 10^{-6} \times 48}{0.1 \times 10.42} = 258 \mu\text{H} \quad (3.1)$$

$$C_o \geq \frac{\Delta I_{Lo} T_s}{8 \Delta V_o} = \frac{1.042 \times 10 \times 10^{-6}}{8 \times 0.24} = 5.43 \mu\text{H} \text{ uF} \quad (3.2)$$

In practice, the output inductor  $L_o=260\mu\text{H}$  and the output capacitor  $C_o=220\mu\text{F}$ . The equivalent series resistances (ESRs) of the output inductor and capacitor are  $R_{Lo}=0.1\Omega$  and  $R_{Co}=0.2\Omega$ , respectively.

#### 3.1.2 Small-Signal Modeling of Buck DC-DC Converter

The operation principle of the Buck converter is simple: when the switch  $S$  is turned-on, the input source  $V_{in}$  supplies power to the load through the output inductor  $L_o$  and output capacitor  $C_o$ , as shown in Fig. 3.2A when  $S$  is turned-off, the inductor  $L_o$  and output capacitor  $C_o$  release energy to the load via the freewheeling diode  $D$ , as shown in Fig. 3.2B. The duty cycle of  $S$  being

 
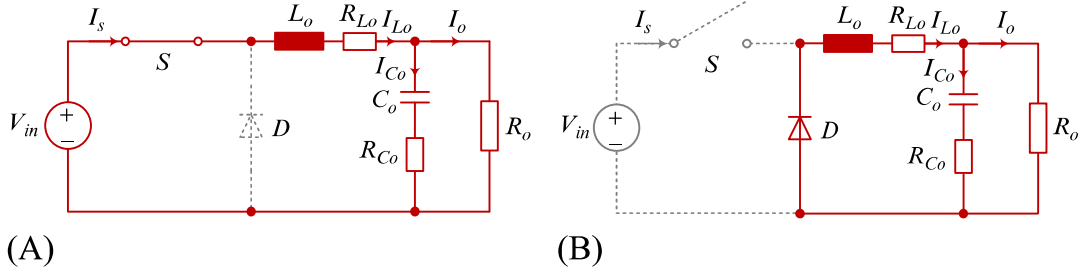


FIG. 3.1 Circuit diagram of the buck DC-DC converter.

FIG. 3.2 Equivalent circuit of the Buck dc-dc converter when the switch  $S$  is (A) turned-on or (B) turned-off.

turned-on is denoted as  $d$  and then that of  $S$  being off is  $1 - d$  if the deadtime is neglected. According to the Kirchhoff's current and Kirchhoff's voltage laws, the basic differential equations can be derived for the two states.

State I ( $t \in [0, dT_s]$ ), switch  $S$  is turned on:

$$\begin{cases} L_o \frac{di_{L_o}}{dt} = v_{in} - v_o - R_{L_o} i_{L_o} \\ C_o \frac{dv_{C_o}}{dt} = i_{L_o} - i_o \\ v_o = v_{C_o} + R_{C_o} (i_{L_o} - i_o) \end{cases} \quad (3.3)$$

State II ( $t \in [dT_s, T_s]$ ), switch  $S$  is turned off:

$$\begin{cases} L_o \frac{di_{L_o}}{dt} = -v_o - R_{L_o} i_{L_o} \\ C_o \frac{dv_{C_o}}{dt} = i_{L_o} - i_o \\ v_o = v_{C_o} + R_{C_o} (i_{L_o} - i_o) \end{cases} \quad (3.4)$$

The time durations for states I and II are  $dT_s$  and  $(1 - d)T_s$ , respectively. In the meanwhile, the state variables (i.e., the inductor current  $i_{L_o}$  and the capacitor voltage  $v_{C_o}$ ) and the output variable (i.e., the output voltage  $v_o$ ) are continuous

in time. Therefore, the averaged differential equations over one switching cycle can be obtained as follows 平均的差分电流在一个PWM开关周期内，连续的

$$\begin{cases} L_o \frac{di_{Lo}}{dt} = dv_{in} - v_o - R_{Lo}i_{Lo} \\ C_o \frac{dv_{Co}}{dt} = i_{Lo} - i_o \\ v_o = v_{Co} + R_{Co}(i_{Lo} - i_o) \end{cases} \quad (3.5)$$

As can be seen from Eq. (3.5) that there is a term  $dv_{in}$  which is a product of the input variable  $v_{in}$  and the control variable  $d$ . That is the averaged model is nonlinear, and therefore the controller cannot be designed with the classical control theory. In order to obtain a linear model, perturbations at the steady-state operation (equilibrium) point should be performed. In this way, each variable contains a DC term (i.e., the steady-state operation point) and a small AC term, i.e.,  $i_{Lo} = I_{Lo} + \tilde{i}_{Lo}$ ,  $v_{Co} = V_{Co} + \tilde{v}_{Co}$ ,  $v_o = V_o + \tilde{v}_o$ ,  $i_o = I_o + \tilde{i}_o$ ,  $v_{in} = V_{in} + \tilde{v}_{in}$ , and  $d = D + \tilde{d}$ . Substituting them into Eq. (3.5) yields

$$\begin{cases} L_o \frac{d}{dt}(I_{Lo} + \tilde{i}_{Lo}) = (D + \tilde{d})(V_{in} + \tilde{v}_{in}) - (V_o + \tilde{v}_o) - R_{Lo}(I_{Lo} + \tilde{i}_{Lo}) \\ C_o \frac{d}{dt}(V_{Co} + \tilde{v}_{Co}) = (I_{Lo} + \tilde{i}_{Lo}) - (I_o + \tilde{i}_o) \\ (V_o + \tilde{v}_o) = (V_{Co} + \tilde{v}_{Co}) + R_{Co}[(I_{Lo} + \tilde{i}_{Lo}) - (I_o + \tilde{i}_o)] \end{cases} \quad (3.6)$$

Applying the steady-state differential equation and neglecting the second-order terms, Eq. (3.6) can be simplified as linear small-signal AC equations

$$\begin{cases} L_o \frac{d}{dt}\tilde{i}_{Lo} = D\tilde{v}_{in} + \tilde{d}V_{in} - \tilde{v}_o - R_{Lo}\tilde{i}_{Lo} \\ C_o \frac{d}{dt}\tilde{v}_{Co} = \tilde{i}_{Lo} - \tilde{i}_o \\ \tilde{v}_o = \tilde{v}_{Co} + R_{Co}(\tilde{i}_{Lo} - \tilde{i}_o) \end{cases} \quad (3.7)$$

Performing Laplace transform to Eq. (3.7) yields its frequency-domain form, i.e.,

$$\begin{cases} sL_o\tilde{i}_{Lo}(s) = D\tilde{v}_{in}(s) + \tilde{d}(s)V_{in} - \tilde{v}_o(s) - R_{Lo}\tilde{i}_{Lo}(s) \\ sC_o\tilde{v}_{Co}(s) = \tilde{i}_{Lo}(s) - \tilde{i}_o(s) \\ \tilde{v}_o(s) = \tilde{v}_{Co}(s) + R_{Co}[\tilde{i}_{Lo}(s) - \tilde{i}_o(s)] \end{cases} \quad (3.8)$$

Eliminate  $v_{Co}(s)$  and  $i_{Lo}(s)$  in Eq. (3.8), and  $\tilde{v}_o(s)$  can be obtained:

$$\tilde{v}_o(s) = \frac{[D\tilde{v}_{in}(s) + V_{in}\tilde{d}(s) - R_{Lo}\tilde{i}_o(s) - sL_o\tilde{i}_o(s)] \cdot (1 + sR_{Co}C_o)}{1 + sC_o(R_{Co} + R_{Lo}) + s^2C_oL_o} \quad (3.9)$$

Then different small-signal transfer functions can be derived with Eq. (3.9)

$$\begin{aligned}
 G_{d2v_o} &= \left. \frac{\tilde{v}_o(s)}{\tilde{d}(s)} \right|_{\tilde{v}_{in}(s)=0, \tilde{i}_o(s)=0} = \frac{V_{in}(1+sR_{C_o}C_o)}{1+sC_o(R_{C_o}+R_{L_o})+s^2C_oL_o} \\
 G_{v_{in}2v_o} &= \left. \frac{\tilde{v}_o(s)}{\tilde{v}_{in}(s)} \right|_{\tilde{d}(s)=0, \tilde{i}_o(s)=0} = \frac{D(1+sR_{C_o}C_o)}{1+sC_o(R_{C_o}+R_{L_o})+s^2C_oL_o} \\
 G_{i_o2v_o} &= \left. \frac{\tilde{v}_o(s)}{\tilde{i}_o(s)} \right|_{\tilde{d}(s)=0, \tilde{v}_{in}(s)=0} = \frac{-(R_{L_o}+sL_o) \cdot (1+sR_{C_o}C_o)}{1+sC_o(R_{C_o}+R_{L_o})+s^2C_oL_o}
 \end{aligned} \tag{3.10}$$

### 3.1.3 Voltage-Model Controller Design of Buck DC-DC Converter

The PI controller can be expressed as

$$G_{PI}(s) = K_p \left( 1 + \frac{K_I}{s} \right) \tag{3.11}$$

The system switching frequency  $\omega_s = 628.32 \text{ krad/s}$ . The bode plot of the control-to-output transfer function is shown in Fig. 3.3. As can be observed,

 


FIG. 3.3 Bode plot of the control-to-output transfer function, the PI controller, and the loop gain.

交叉点

there are two corner frequencies, 4.21 and 8.35 krad/s, and the crossover frequency is 167 krad/s. In the meanwhile, the crossover frequency of the open-loop transfer function should not be higher than 1/10 to 1/5 of the switching frequency. In this case, the crossover  $\omega_c$  is set as 1/9 of the switching frequency, i.e.,  $\omega_c$  should be corrected to be about 69.8 krad/s.

The gain of the control-to-output transfer function at  $\omega_c = 69.8$  krad/s is 7.69 dB. Therefore, the required gain from the PI compensator should be  $K_p = -7.69$  dB = 0.4126. The corner frequency of the PI controller should approximately correspond to the first corner frequency of the control-to-output transfer function. Thus,  $K_I = \omega_I = 4.21$  krad/s.

The transfer functions of both the PI controller and the open-loop gain are depicted in Fig. 3.3 as well. As can be seen, the open-loop transfer function has been corrected with the crossover frequency  $\omega_c = 69.8$  krad/s and the phase margin being equal to  $80^\circ$ . The bode plots of open-loop and closed-loop transfer functions are shown in Fig. 3.4. It can be observed that the high loop gain results in a strong suppression of disturbances.

### 3.1.4 Simulation Results of the Case Study

电路仿真和小信号建模仿真


The closed-loop results from the circuit simulation and the small-signal model are shown in Figs. 3.5–3.7. Both the analytical modeling and simulation results are based on the specific case study described in Section 3.1.1. As can be seen, the developed small-signal model and the designed controller can predict both the dynamic and static performances of the Buck DC-DC converter with negligible error compared to simulations. When the output voltage reference is changed from 48 to 49 V, the PI controller helps the system to track the reference tightly, as shown in Fig. 3.5. When the perturbations (i.e., the input voltage in Fig. 3.6 and the load in Fig. 3.7) appear, their impact on the output voltage can be effectively attenuated.

## 3.2 FREQUENCY-DOMAIN CURRENT-MODE CONTROL OF A BOOST DC-DC CONVERTER

### 3.2.1 Specifications of the Boost DC-DC Converter

额定负载是61.25  $\Omega$ 

The circuit diagram of a current mode-controlled (CMC) Boost DC-DC converter is shown in Fig. 3.8. The input voltage  $v_i = 150$  V, the output voltage  $v_o = 350$  V, the nominal output power  $P_o = 2$  kW, the switching frequency  $f_s = 50$  kHz, and the maximum current ripple in the input inductor  $L$  is limited to 25%. An inductor with inductance  $L = 514$   $\mu$ H and ESR  $R_L = 0.02$   $\Omega$  is selected. The output capacitor  $C = 450$   $\mu$ F and its ESR  $R_C = 0.01$   $\Omega$ . The current sensor resistor  $R_s$  shown in Fig. 3.8 is 0.2  $\Omega$ .

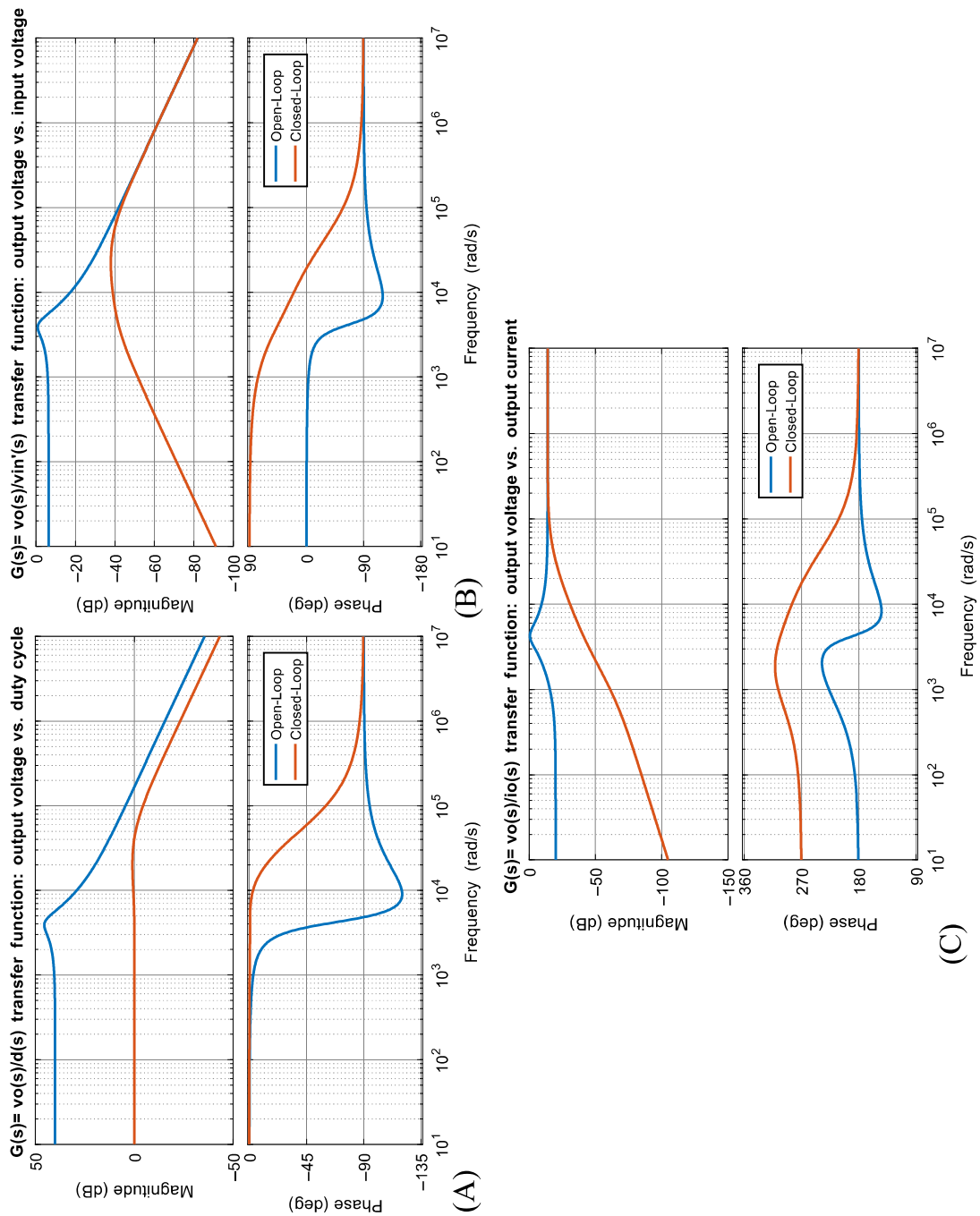

**FIG. 3.4** Bode plot of open-loop and closed-loop transfer functions. (A) Control-to-output transfer function, (B) input-to-output transfer function, and (C) output impedance.

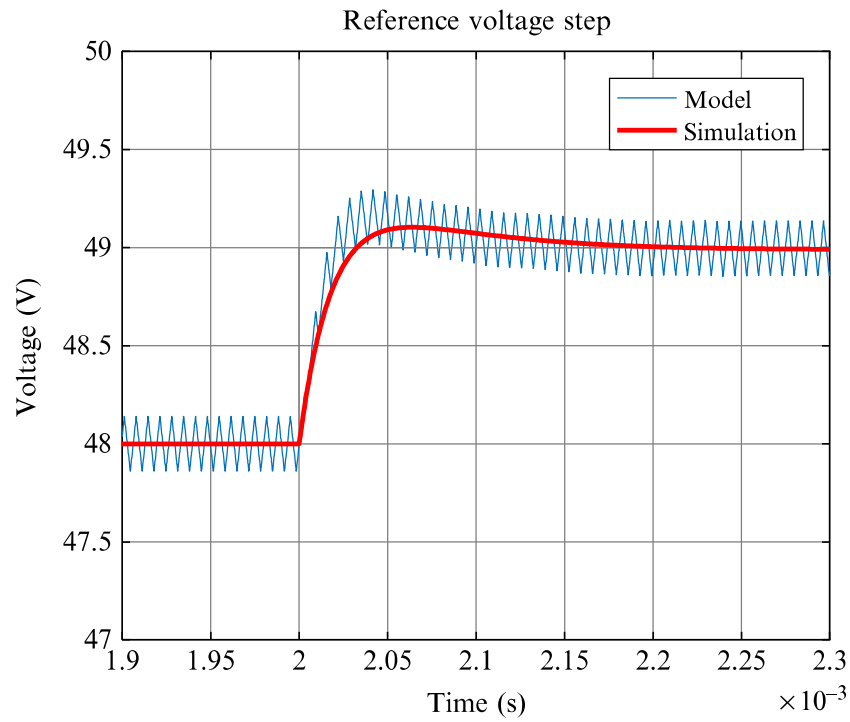


FIG. 3.5 The output voltage reference is varied from 48 to 49 V.

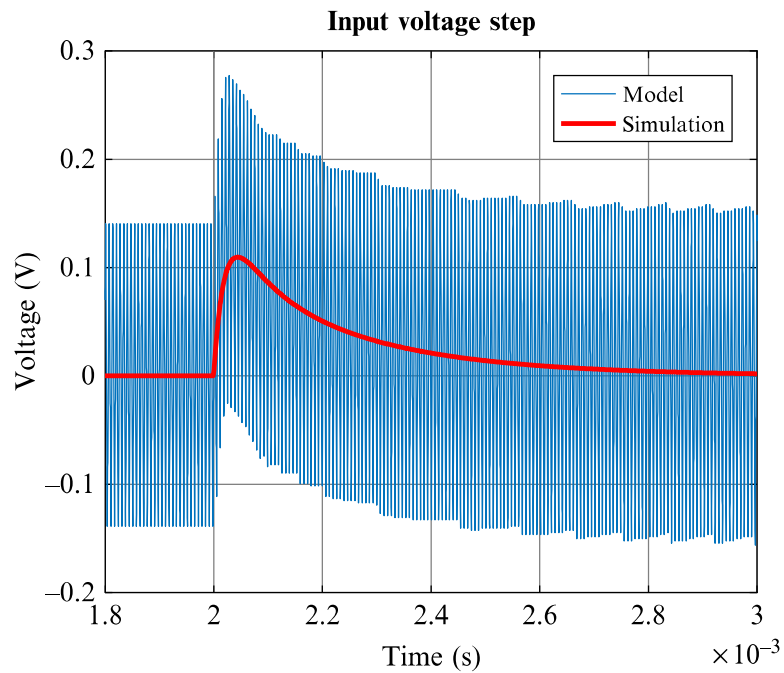


FIG. 3.6 The input voltage is step-changed from 100 to 110 V at 2 ms.

### 3.2.2 Small-Signal Modeling of Boost DC-DC Converter

Suppose the Boost converter is operating in the **continuous current mode (CCM)**. When  $S$  is turned on, the state equations are

电流连续模式

 


FIG. 3.7 The load is changed from 20 to 10 A at 2 ms.

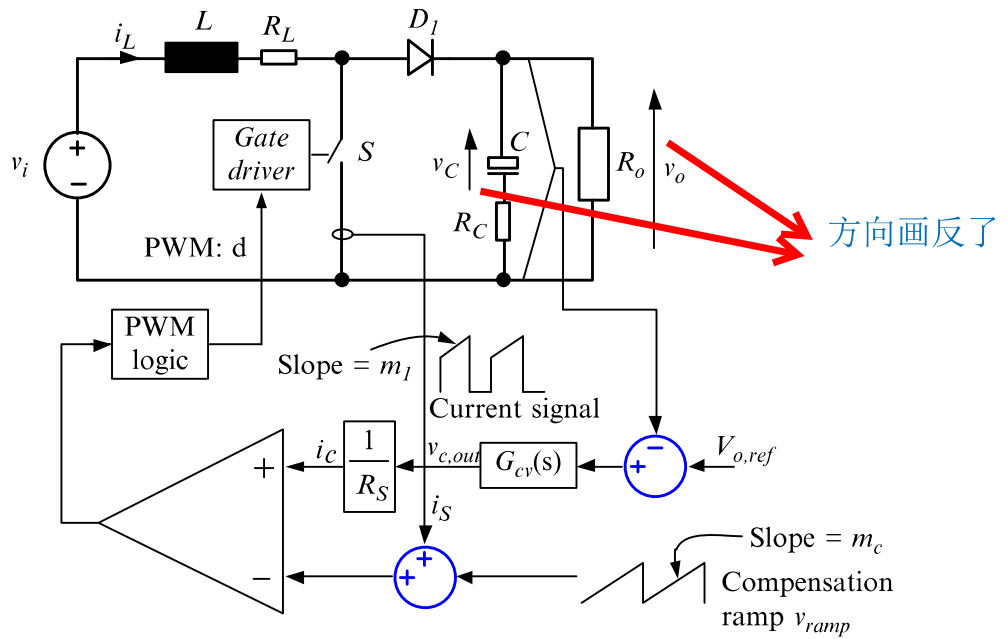


FIG. 3.8 A boost converter with current-mode control.

$$\begin{cases} L \frac{d}{dt} i_L = v_i - i_L R_L \\ C \frac{d}{dt} v_C = -\frac{v_o}{R_o} \end{cases} \quad (3.12)$$

When  $S$  is turned off, the diode  $D_1$  is freewheeling; then the state equations are



$$\begin{cases} L \frac{d}{dt} i_L = v_i - i_L R_L - v_o \\ C \frac{d}{dt} v_C = i_L - \frac{v_o}{R_o} \end{cases} \quad (3.13)$$

According to Eqs. (3.12), (3.13), the average model can be obtained as,

$$\begin{cases} L \frac{d}{dt} \bar{i}_L = \bar{v}_i - \bar{i}_L R_L - (1 - \bar{d}) \bar{v}_o \\ C \frac{d}{dt} \bar{v}_C = (1 - \bar{d}) \bar{i}_L - \frac{\bar{v}_o}{R_o} \end{cases} \quad (3.14)$$

where  $d$  is the duty ratio of the boost converter, and  $\bar{x}$  is the average value of  $x$  ( $x = i_L, v_i, d, v_o, v_C$ ) in a switching cycle. As seen in Fig. 3.8, it is easy to acquire

$$\bar{v}_o = \bar{v}_C + R_C C \frac{d}{dt} \bar{v}_C \quad (3.15)$$

Then, by applying small signal perturbations to Eqs. (3.14), (3.15), it is gained

$$\begin{cases} L \frac{d}{dt} (\bar{I}_L + \tilde{i}_L) = (\bar{V}_i + \tilde{v}_i) - (\bar{I}_L + \tilde{i}_L) R_L - (1 - \bar{D} - \tilde{d}) (\bar{V}_o + \tilde{v}_o) \\ C \frac{d}{dt} (\bar{V}_C + \tilde{v}_C) = (1 - \bar{D} - \tilde{d}) (\bar{I}_L + \tilde{i}_L) - \frac{\bar{V}_o + \tilde{v}_o}{R_o} \\ \bar{V}_o + \tilde{v}_o = \bar{V}_C + \tilde{v}_C + R_C C \frac{d}{dt} (\bar{V}_C + \tilde{v}_C) \end{cases} \quad (3.16)$$

Extract the DC items in Eq. (3.16), it is obtained

$$\begin{cases} 0 = \bar{V}_i - \bar{I}_L R_L - (1 - \bar{D}) \bar{V}_o \\ 0 = (1 - \bar{D}) \bar{I}_L - \frac{\bar{V}_o}{R_o} \\ \bar{V}_o = \bar{V}_C \end{cases} \quad (3.17)$$

By removing the DC and high-order AC items in Eq. (3.16), it is acquired

$$\begin{cases} L \frac{d}{dt} \tilde{i}_L = \tilde{v}_i - \tilde{i}_L R_L - (1 - \bar{D}) \tilde{v}_o + \tilde{d} \bar{V}_o \\ C \frac{d}{dt} \tilde{v}_C = (1 - \bar{D}) \tilde{i}_L - \tilde{d} \bar{I}_L - \frac{\tilde{v}_o}{R_o} \\ \tilde{v}_o = \tilde{v}_C + R_C C \frac{d}{dt} \tilde{v}_C \end{cases} \quad (3.18)$$

By performing Laplace transform to Eq. (3.18), it is obtained

$$\begin{cases} sL\tilde{i}_L(s) = \tilde{v}_i(s) - \tilde{i}_L(s)R_L - (1-\bar{D})\tilde{v}_o(s) + \tilde{d}(s)\bar{V}_o \\ sC\tilde{v}_C(s) = (1-\bar{D})\tilde{i}_L(s) - \tilde{d}(s)\bar{I}_L - \frac{\tilde{v}_o(s)}{R_o} \\ \tilde{v}_o(s) = \tilde{v}_C(s) + sR_C C\tilde{v}_C(s) \end{cases} \quad (3.19)$$

Then, Eq. (3.20) can be derived from Eq. (3.19), and the control to output voltage transfer function of the open-loop boost converter is obtained as shown in Eq. (3.21).

$$\tilde{v}_o(s) = \frac{\frac{1+sR_C C}{1-\bar{D}}\tilde{v}_i(s) + \frac{1+sR_C C}{(1-\bar{D})^2}\bar{V}_i \left[ 1 - \frac{sL}{R_o(1-\bar{D})^2} \right] \tilde{d}(s)}{s^2 \frac{LC}{(1-\bar{D})^2} + s \left[ \frac{L+R_L R_o C}{R_o(1-\bar{D})^2} + R_C C \right] + 1} \quad (3.20)$$

$$G_{d2v_o} = \frac{\tilde{v}_o(s)}{\tilde{d}(s)} \bigg|_{\tilde{v}_i(s)=0} = \frac{\frac{1+sR_C C}{(1-\bar{D})^2}\bar{V}_i \left[ 1 - \frac{sL}{R_o(1-\bar{D})^2} \right]}{s^2 \frac{LC}{(1-\bar{D})^2} + s \left[ \frac{L+R_L C}{(1-\bar{D})^2} + R_C C \right] + 1} \quad (3.21)$$

Fig. 3.9 shows the peak current control of the boost converter, where the switch current  $i_s$  instead of the inductor current  $i_L$  is applied to compare with the reference  $i_c$  that is generated by the voltage compensator. Moreover, in order to increase the damping and mitigate the subharmonic caused by the peak current control, a slope  $m_c$  is added into  $i_s$  before compared with  $i_c$ , as illustrated in Figs. 3.8 and 3.9. The design of  $m_c$  will be demonstrated in the following section. By solving the simple trigonometry in Fig. 3.9, it is obtained

$$\bar{i}_L = i_c - m_c \bar{d}T_s - \frac{m_1}{2} \bar{d}T_s \quad (3.22)$$

$$m_1 = \frac{v_i}{L} \quad (3.23)$$

 


FIG. 3.9 The schematic diagram of peak current control.

By substituting Eq. (3.23) and then applying small-signal perturbation to Eq. (3.22), it is acquired

$$\bar{I}_L + \tilde{i}_L = \bar{I}_c + \tilde{i}_c - m_c (\bar{D} + \tilde{d}) T_s - \frac{\bar{V}_i + \tilde{v}_i}{2L} (\bar{D} + \tilde{d}) T_s \quad (3.24)$$

By removing the DC and high-order AC components in Eq. (3.24), it is gained

$$\tilde{i}_L = \tilde{i}_c - m_c \tilde{d} T_s - \frac{\bar{V}_i \tilde{d} + \bar{D} \tilde{v}_i}{2L} T_s \quad (3.25)$$

By performing Laplace transformation to Eq. (3.25), it is obtained

$$\tilde{i}_L(s) = \tilde{i}_c(s) - m_c \tilde{d}(s) T_s - \frac{\bar{V}_i \tilde{d}(s) + \bar{D} \tilde{v}_i(s)}{2L} T_s \quad (3.26)$$

According to Eqs. (3.19), (3.26), it can be acquired

$$\tilde{v}_o(s) = \frac{G_{NC}(s) \tilde{v}_i(s) + G_{IC}(s) \tilde{i}_c(s)}{\Delta(s)} \quad (3.27)$$

where

$$G_{NC}(s) = (1 - \bar{D}) R_o \left[ \frac{s \bar{D} T_s}{2(1 - \bar{D})^2 R_o} + \frac{1}{(1 - \bar{D})^2 R_o} - \frac{\bar{D} T_s}{2L} + \left( 1 + \frac{2m_c}{\bar{V}_i} \right) \frac{(1 - \bar{D}) T_s}{2} \right] \quad (3.28)$$

$$G_{IC}(s) = (1 - \bar{D}) R_o (1 + s R_C C) \left[ 1 - \frac{sL}{(1 - \bar{D})^2 R_o} \right] \quad (3.29)$$

$$\begin{aligned} \Delta(s) = & s^2 L (R_o + R_C) C (1 - \bar{D}) \left( \frac{m_c}{\bar{V}_i} + \frac{1}{2L} \right) T_s \\ & + s \left\{ \left[ L + (1 - \bar{D})^2 R_o R_C C \right] (1 - \bar{D}) \left( \frac{m_c}{\bar{V}_i} + \frac{1}{2L} \right) T_s + (R_o + 2R_C) C \right\} \\ & + 2 + (1 - \bar{D})^2 R_o (1 - \bar{D}) \left( \frac{m_c}{\bar{V}_i} + \frac{1}{2L} \right) T_s \end{aligned} \quad (3.30)$$

Assuming that the switch current is sampled via a resistor  $R_S$ , or the equivalent resistance of the current sensor is  $R_S$ , the control to output voltage transfer function of the boost converter with current mode control is obtained

$$G_{v_c, out 2v_o} = \frac{\tilde{v}_o(s)}{\tilde{v}_{c, out}(s)} \bigg|_{\tilde{v}_i(s)=0} = \frac{G_{IC}(s)}{\Delta(s) R_S} \quad (3.31)$$

### 3.2.3 Current-Model Controller Design of Boost DC-DC Converter

A typical issue brought by peak current control is the subharmonics resonance, and it is indicated in Fig. 3.10. As seen, with an improperly designed  $m_c$ , the

 


FIG. 3.10 Subharmonic resonance in current mode-controlled boost converter.

inductor current disturbance  $\Delta i_{L,0}$  can be amplified after two switching cycles. The impact of  $m_c$  on the subharmonics resonance can be revealed by solving the trigonometry in Fig. 3.10, and it is obtained

$$\frac{\Delta i_{L,0}}{AB} = \frac{EF}{AF}, \quad \frac{EF}{FH} = \frac{-\Delta i_{L,1}}{QH} \quad (3.32)$$

Merge the two equations in Eq. (3.32), and it is acquired

$$\Delta i_{L,1} = -\frac{QH AF}{AB FH} \Delta i_{L,0} = -\frac{m_1 \bar{d} T_s - m_c (1 - \bar{d}) T_s}{(m_1 + m_c) \bar{d} T_s} \frac{\bar{d}}{1 - \bar{d}} \Delta i_{L,0} \quad (3.33)$$

To avoid the subharmonics resonance, it requires

$$|\Delta i_{L,1}| \leq |\Delta i_{L,0}| \quad (3.34)$$


Substitute Eq. (3.33) into Eq. (3.34), it is gained

$$\frac{m_1 \bar{d} T_s - m_c (1 - \bar{d}) T_s}{(m_1 + m_c) \bar{d} T_s} \frac{\bar{d}}{1 - \bar{d}} \leq 0.5 \Rightarrow m_c \geq m_1 \frac{2\bar{d} - 1}{2(1 - \bar{d})} \quad (3.35)$$

Since the minimum value of  $m_c$  is zero, the condition to eliminate subharmonics resonance is obtained as Eq. (3.36) by substituting Eq. (3.23) into Eq. (3.35).

$$m_c \geq \begin{cases} 0, & \bar{d} \leq 0.5 \\ \frac{v_i}{L} \frac{2\bar{d} - 1}{2(1 - \bar{d})}, & \bar{d} > 0.5 \end{cases} \quad (3.36)$$

A voltage compensator is designed in this section for a current mode controlled boost converter with the specifications described in Section 3.2.1. Substitute the parameter values into Eq. (3.21), and the characteristics of the transfer function  $G_{d2v_o}$  is obtained as below:

 

**FIG. 3.11** Frequency response of the open-loop boost converter.

DC gain: 4083

Poles:  $-39.4 \pm 890j$  rad/s

Zeros:  $-2.2 \times 10^5$  rad/s,  $2.19 \times 10^4$  rad/s (Right-Half-Plane, RHP)

Fig. 3.11 shows the frequency response of the open-loop-controlled Boost converter. As seen, the open-loop system has a resonant point, where the phase is decreased sharply to  $-180^\circ$ . Thus, if a voltage mode control is applied, a much lower crossover frequency than the resonant frequency is necessary for the voltage compensator to damp the resonance and make the system stable.

Substitute the parameter values into Eq. (3.31), the characteristics of the transfer function  $G_{v_{c,out}2VO}$  are obtained:

DC gain: 62

Poles:  $-80$  rad/s,  $-1.67 \times 10^5$  rad/s

Zeros:  $-2.2 \times 10^5$  rad/s,  $2.19 \times 10^4$  rad/s (RHP)


Crossover frequency:  $4.9 \times 10^3$  rad/s

Phase margin:  $78^\circ$

where  $m_c$  is set as Eq. (3.37) according to the subharmonics resonance mitigation condition in Eq. (3.36), and a 20% safety margin is applied.

$$m_c = 1.2 \frac{v_i}{L} \frac{2\bar{d} - 1}{2(1 - \bar{d})} \quad (3.37)$$

Fig. 3.12 shows the frequency response of the uncompensated boost converter with current-mode control. As seen, the resonant point does not exist

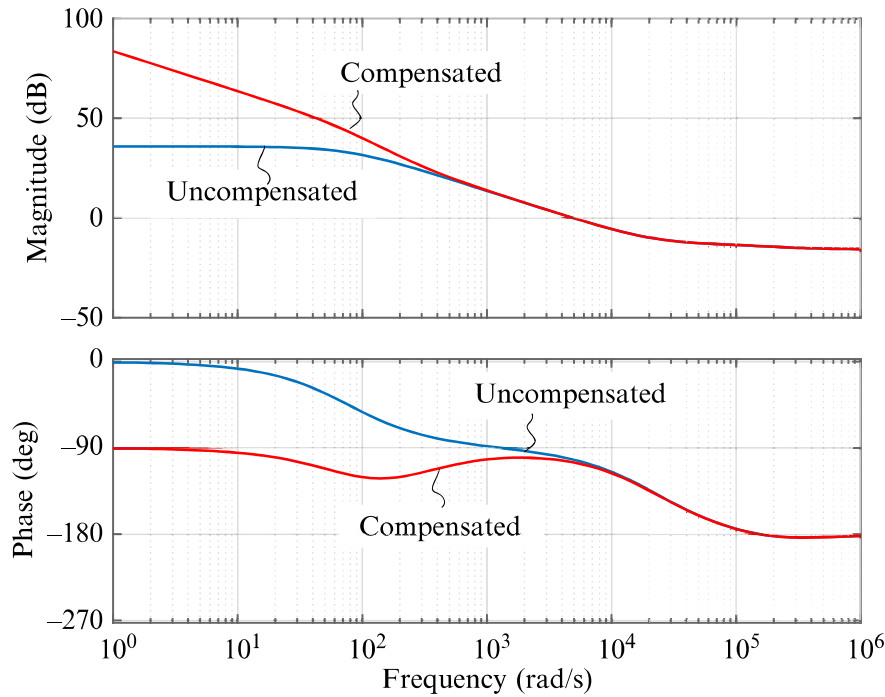

**FIG. 3.12** Frequency responses of the current-model-controlled boost converter with and without compensation.

无限的

any more compared with Fig. 3.11. To realize an infinite DC gain for nonzero steady-state error tracking, a proportional + integral (PI) voltage compensator is used, as shown

$$G_{cv}(s) = K_p \frac{s + \frac{K_i}{K_p}}{s} \quad (3.38)$$

The crossover frequency of the uncompensated system is  $4.9 \times 10^3$  rad/s which is around 1/64 of the switching frequency (50kHz). Normally, the crossover frequency can be set to around 1/10 of the switching frequency to have a reasonably high bandwidth. Therefore, the PI compensator can be designed to increase the crossover frequency of the system. But the uncompensated system has a  $-7$  dB constant gain and  $-180^\circ$  phase at high-frequency band due to the RHP zero, and the corner frequency to the high-frequency band is  $2.19 \times 10^4$  rad/s (RHP zero) which is only four times the crossover frequency. Thus, if the crossover frequency is increased by the PI compensator, then the gain at the high-frequency band will also be increased and thereby the system may lose its stability. It is decided to keep the crossover frequency and phase margin of the system by setting a 0-dB gain at the high-frequency band in the PI compensator. Thus, we can obtain  $K_p = 1$ .

As known, the PI compensator will have a  $-45^\circ$  phase at its corner frequency. To avoid a significant influence on the phase margin of the system, the corner frequency of the PI compensator is set to 1/15 of the crossover frequency of the system, i.e.,

$$K_i/K_p = 4.9/15 \text{ krad/s} \quad (3.39)$$

Thus, it is gained  $K_i = 327$  and


$$G_{cv}(s) = 1 + \frac{327}{s} \quad (3.40)$$

### 3.2.4 Simulation Results of the Case Study

Figs. 3.13 and 3.14 show the simulation results of the specific case study. Without the slope compensations, subharmonics appear when  $m_c$  is equal to  $0.8m_{c0}$ . By adding a slope compensation, the subharmonics can be eliminated. The overshoot and undershoot of the Boost converter output voltage is limited to a relatively low level under step load changes occur, as shown in Fig. 3.14. The results imply a proper current controller for the Boost converter is achieved.

## 3.3 TIME-DOMAIN CONTROL OF BASIC DC-DC CONVERTERS

The controllers of DC-DC converters are dominantly designed with small-signal linearization techniques in frequency domain, as discussed in Sections 3.1 and 3.2. However, DC-DC converters with PWM switching are highly nonlinear systems, and their large-signal characteristics will behave differently from that predicted by small-signal design approaches. To overcome the limitations, various time-domain control methods have been proposed. One major class of them is the switching surface control (i.e., boundary control). The concept is to determine the time sequence to turn on/off switches according to certain constraints, namely, switching surfaces [1]. This section is dedicated to a case study to illustrate the basic concept of a generic second-order boundary

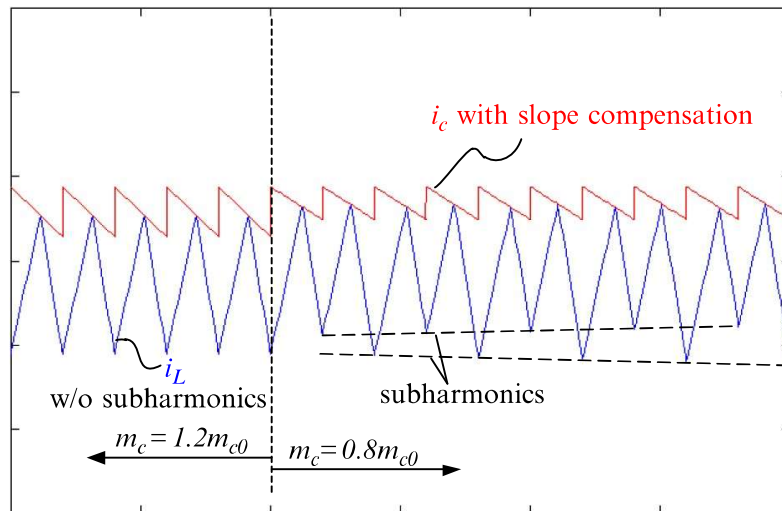

**FIG. 3.13** Simulation results to show the impact of the slope compensation on the subharmonics resonance in peak current control  $\left(m_{c0} = \frac{v_i}{L} \frac{2\bar{d}-1}{2(1-\bar{d})}\right)$ .

 


FIG. 3.14 Simulation results to show the dynamic performance of the system during load step.

control method that can be applicable to both Buck-type (i.e., minimum phase system) and Boost type (i.e., nonminimum phase system) converters. Parts of this section are based on what have been discussed in Ref. [1]. The following discussions are based on a specific example of Buck-Boost converter. It should be noted that the method is applicable to all kinds of basic DC-DC converters (i.e., Buck converter, Boost converter, Buck-Boost converter, Ćuk converter, and SEPIC).

### 3.3.1 Specifications of the Buck-Boost DC-DC Converter

Fig. 3.15 shows the circuit diagram of a Buck-Boost converter. In a specific case study, the parameters are as: output power 190 W, input voltage  $v_{in} = 48$  V, and

 


FIG. 3.15 Circuit diagram of a Buck-Boost converter.